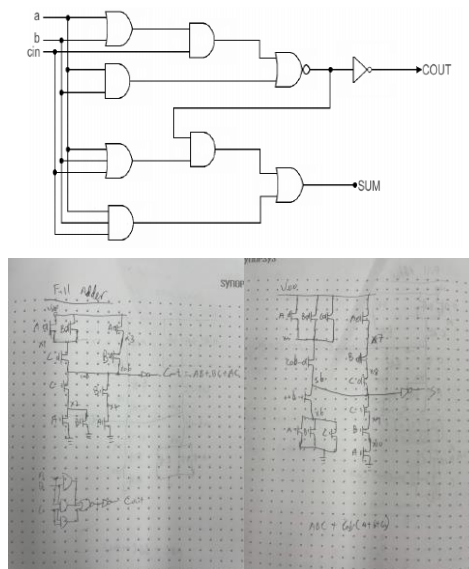



黃偉祥 X1136010

Full Adder




- I use the online Full adder version to design my full adder.
- For Multiple bits full adder, I just connect them together.

D Latch

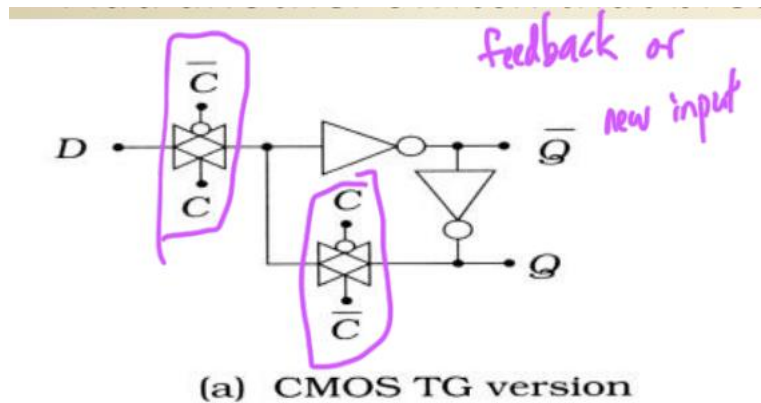


- I use ppt version of D Latch to design my DLatch_TG
- I use D-latch to store Weights.

D Flip Flop

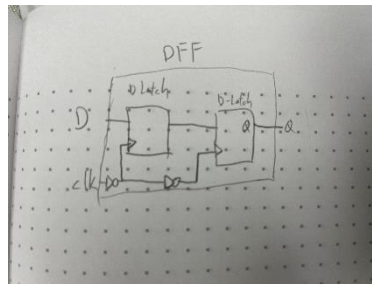

- I use 2 D-latch to build my positive edge DFF

IdotW

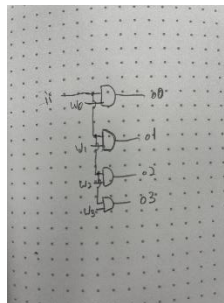

- I just and ii with all w0, w1, w2, w3 separately.
- This use for every I * W in all column and row.


OUT_NOW

- I use 1 DFF to keep the previous IN_VAL, then check if previous IN_VAL is 1 and current IN_VAL is 0 → Fall occurs.
- When Fall occurs then OUT_VAL need to be 1 for a cycle in the next cycle, so I use another DFF to output the OUT_VAL.

CON_IN & CON_OUT

- I use DFF to done this 2, the different is only CON_IN use IN_VAL to check while CON_OUT use RST to check.
- And CON_IN use 4 DFF while CON_OUT use 10 DFF.


Design

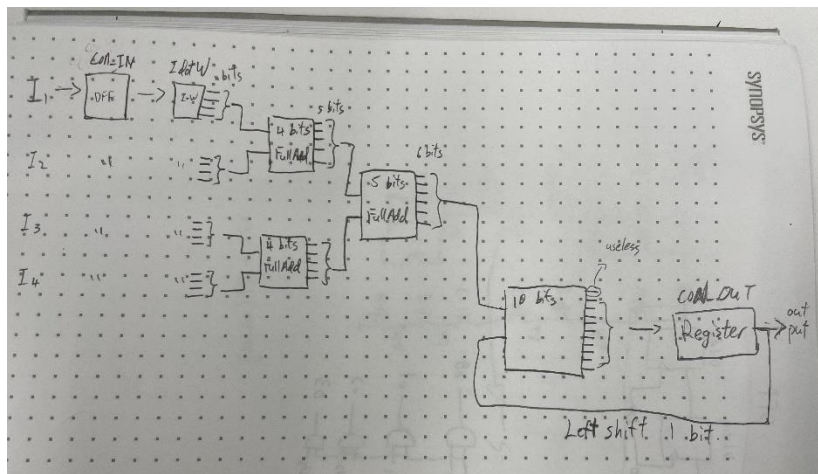


- I use all subcircuit that I show in above and connect them just like the figure above.

Waveform

1. Column 1 wave form

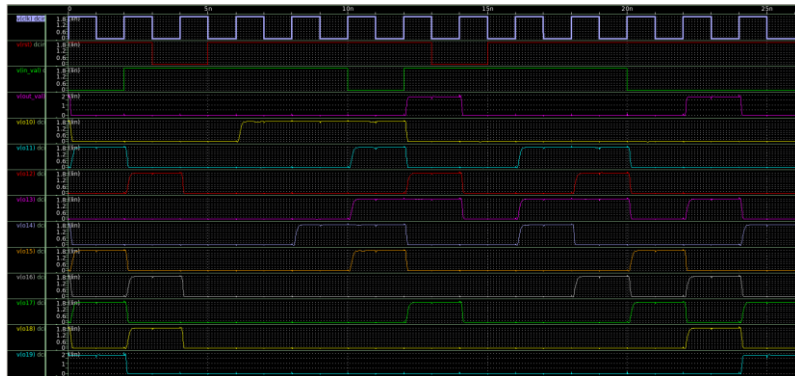

2. Column 2 wave form

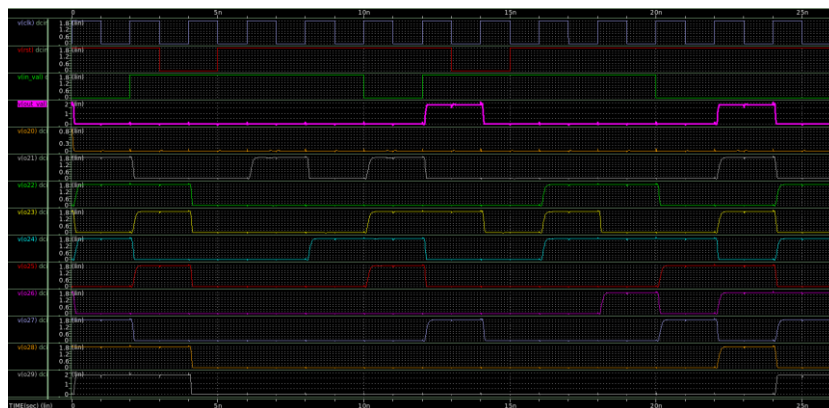

Delay and Power

```
***** transient analysis tnom= 25.000 temp= 30.000 *****
td= 624.0792p targ= 4.8206n trig= 4.1965n
pwr= 1.6866m from= 0. to= 26.0000n

***** job concluded
```

1. Delay = 624.0792 p
2. Power= 1.6866 m

Transistors

```
***** Circuit Statistics *****
# nodes      = 6232 # elements   = 2534
# resistors  = 0 # capacitors = 0 # inductors   = 0
# mutual_inds = 0 # vccs       = 0 # vcvs       = 0
# cccs       = 0 # ccvs       = 0 # volt_srcs  = 8
# curr_srcs  = 0 # diodes    = 0 # bjts       = 0
# jfets      = 0 # mosfets   = 2526 # U elements = 0
# T elements = 0 # W elements = 0 # B elements = 0
# S elements = 0 # P elements = 0 # va device  = 0
# vector_srcs = 0 # N elements = 0
```

- Total : 2526 mosfets

Bonus

```
***** Circuit Statistics *****
# nodes      = 428942 # elements   = 173192
# resistors  = 0 # capacitors = 0 # inductors   = 0
# mutual_inds = 0 # vccs       = 0 # vcvs       = 0
# cccs       = 0 # ccvs       = 0 # volt_srcs  = 8
# curr_srcs  = 0 # diodes    = 0 # bjts       = 0
# jfets      = 0 # mosfets   = 173184 # U elements = 0
# T elements = 0 # W elements = 0 # B elements = 0
# S elements = 0 # P elements = 0 # va device  = 0
# vector_srcs = 0 # N elements = 0
```

- Total 173184 Mosfets

- Design

DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2
DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2
DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2
DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2
DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2
DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2
DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2
DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2	DCIM4_2

- I use the basic DCIM4_2 to build a DCIM32_2
 - ◆ DCIM4_2 is the DCIM in basic part
 - ◆ DCIM32_2 have 32 rows and 2 columns
- Then I use 8 * DCIM32_2 to build DCIM
 - ◆ This DCIM will take Input I1~I32, and output O10~O169
 - Total 32 inputs
 - Total 160 outputs
 - Each DCIM32_2 will produce 20 outputs * 8 DCIM32_2
- Weights is a bit different with basic, which can just for all column with same weight, so I set weights inside DCIM circuit
 - ◆ $Xw1 \sim Xw16$
- Then pass it to DCIM32_2 separately and initial it using .ic
 $V(Xdcim.Xwx.wx)=xv$

Hardness

1. The Full adder delay of my design, this gives me so much trouble when checking problem and debugging.
 - 甲、Thanks my friend helping me to get another kind of Full adder design and then everything done!
2. First I thought Latch and Flip-flop is the same thing, but then when TA time I knew that we need to use flip-flop instead of latch...
 - 甲、TQ TA, I will check the document properly next time...
3. I need more TA time and my email always get into dustbin...