



CS3120

Introduction of Integrated Circuit Design



Homework 2: Layout Design

Andy, Yu-Guang Chen

Associate Professor, Department of EE, National Central University

Adjunct Assistant Professor, Department of CS, National Tsing Hua University

andygchen@ee.ncu.edu.tw

Slides Credit: TA 張孫婕



2024/11/5

Andy Yu-Guang Chen

1



Outline

- ◆ Description
- ◆ Input/Output
- ◆ Report
- ◆ Grading
- ◆ DRC Rules
- ◆ Notice





Outline


- ◆ **Description**
- ◆ **Input/Output**
- ◆ **Report**
- ◆ **Grading**
- ◆ **DRC Rules**
- ◆ **Notice**





Description

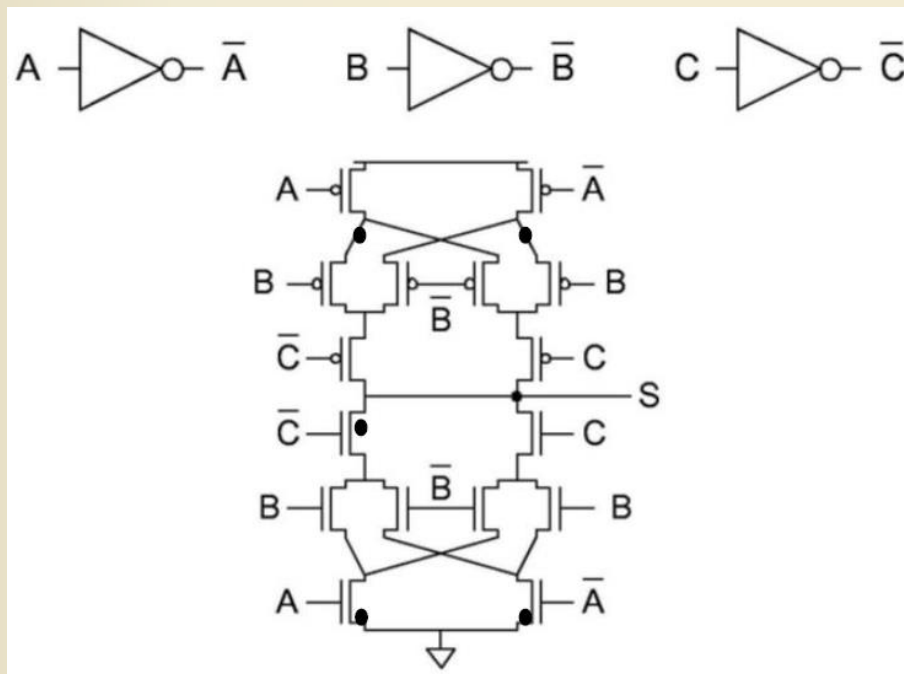- ◆ Design a 3-input XOR gate which drives a capacitance of 0.005pF
- ◆ Use the design form in the document





Description

- ◆ Operating voltage (V_{DD}): 1.8V
- ◆ Operating temperature: 30°C
- ◆ Capacitive of output S is 0.005pF
- ◆ For transistors
 - set $L = 0.18\mu\text{m}$
 - The minimum value of W is $0.25\mu\text{m}$, and the value of W can be adjusted as needed





Outline

- ◆ Description
- ◆ **Input/Output**
- ◆ Report
- ◆ Grading
- ◆ DRC Rules
- ◆ Notice





Input/Output

- ◆ The input should include the combinations of $(C, B, A) = (0, 0, 0), (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1), (1, 1, 0)$ and $(1, 1, 1)$ in sequence
- ◆ The naming and pinouts of each input and output must match the figures provided in the document





Input/Output

◆ Input signals:

- 50% duty cycle
- A operates at 200 MHz, B at 100 MHz, and C at 50 MHz
- The order of input combinations (C, B, A) should match the orders in the document
- Set rise/fall time of the input signals to 10ps





Input/Output

◆ Output signals:

- Highest voltage must be larger than $0.9V_{DD}$
- Lowest voltage must be lower than $0.1V_{DD}$





Input/Output

- ◆ Need to show the delay and the difference in delay between rising and falling delay in the 3-input XOR gate
 - Delay1_XOR: signal A and S are falling
 - Delay2_XOR: signal A and S are rising
 - $| \text{Delay1_XOR} - \text{Delay2_XOR} | = \underline{\hspace{2cm}} \text{ ps}$





Outline

- ◆ Description
- ◆ Input/Output
- ◆ **Report**
- ◆ Grading
- ◆ DRC Rules
- ◆ Notice





Report

1. The circuit diagram of your design and explaining your design
2. Pre-sim waveform
3. Screenshot of your layout
4. Screenshot of DRC summary report
5. Screenshot of LVS report include the message of passing LVS





Report

6. Post-sim waveform
7. Screenshot of the post-simulation result
8. Write down your delay and the difference in delay between rising and falling delay in the 3-input XOR gate
9. The hardness of this assignment and how you overcome it
10. Any suggestions about this programming assignment





Outline

- ◆ Description
- ◆ Input/Output
- ◆ Report
- ◆ **Grading**
- ◆ DRC Rules
- ◆ Notice





Grading

- ◆ Correctness: 40%
 - Pre-sim: 10%
 - DRC: 10%
 - LVS: 10%
 - Post-sim: 10%
- ◆ Performance: power, area 10%
- ◆ Readability of hspice code: 10%
- ◆ Report: 10%
- ◆ Demo session: 30%
- ◆ Bonus: 10%





Outline

- ◆ Description
- ◆ Input/Output
- ◆ Report
- ◆ Grading
- ◆ **DRC Rules**
- ◆ Notice






DRC Rules

- ◆ cont width and length = $0.23\mu\text{m}$
- ◆ Spacing between cont and diff $> 0.12\mu\text{m}$
- ◆ Spacing between Pimp/Nimp and diff $> 0.2\mu\text{m}$
- ◆ Spacing between poly and cont $> 0.14\mu\text{m}$
- ◆ Spacing between metal and metal $> 0.24\mu\text{m}$
- ◆ Spacing between cont and cont $> 0.25\mu\text{m}$






DRC Rules

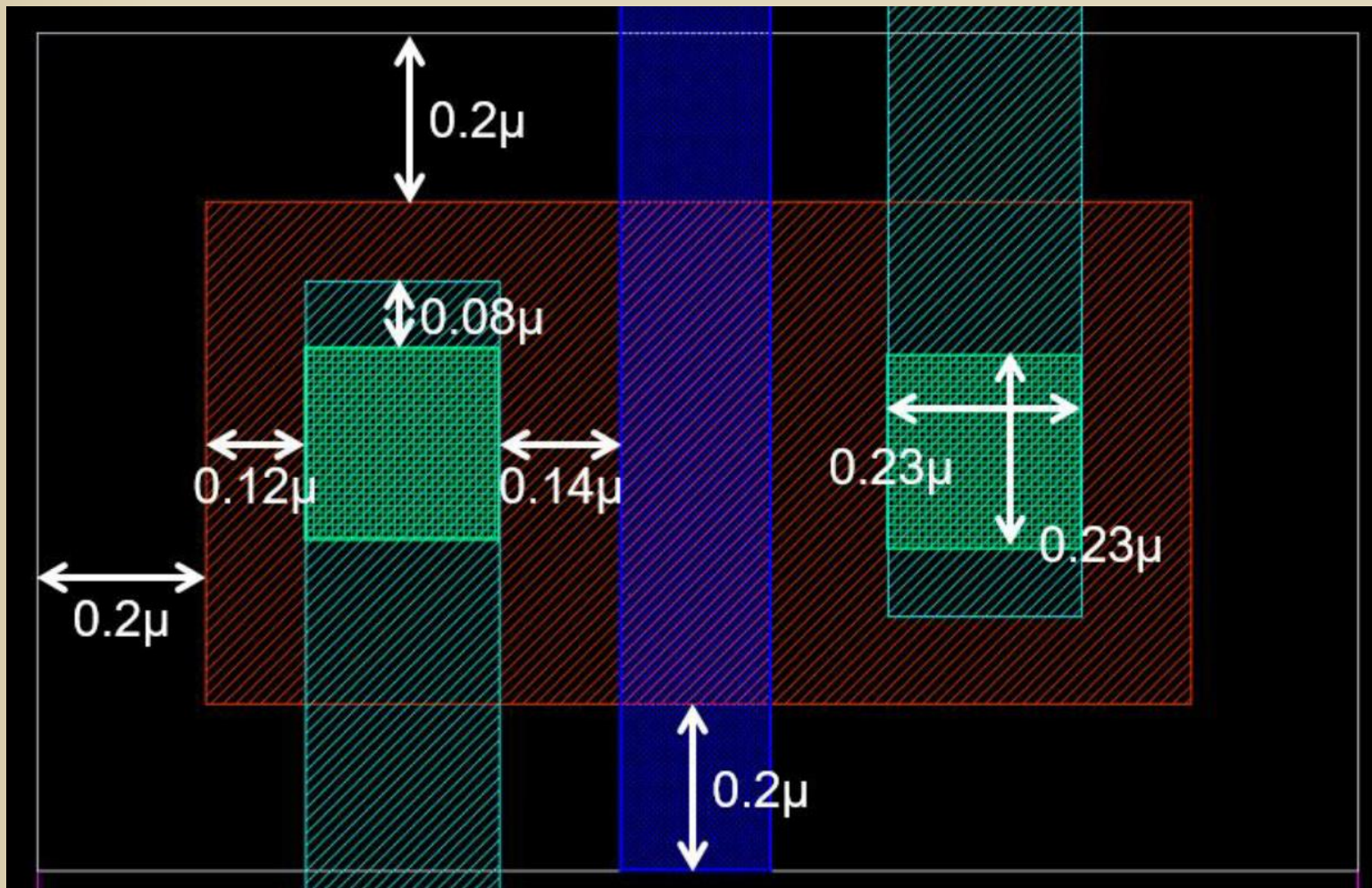



DRC Rules

 - ◆ The length of W is determined by your design
 - Will compare with the HSPICE code when you run LVS
- ◆ The W and L in your layout must be the same as the ones in HSPICE code





Outline

- ◆ Description
- ◆ Input/Output
- ◆ Report
- ◆ Grading
- ◆ DRC Rules
- ◆ **Notice**





Notice

- ◆ Only Metal 1 、 Metal 2 and Via can be used when routing
- ◆ You must use the same approach as 'cic018.l' and 'cic18.tf' in HW2 to do this assignment; otherwise, you will get 0 points
- ◆ BE SURE to follow the naming rule in the document; otherwise, your program will not be graded

