



CS3120

Introduction of Integrated Circuit Design



Final Project

Andy, Yu-Guang Chen

National Tsinghua University

andygchen@ee.ncu.edu.tw

Presented by TA 施奕瑄



2024/12/6

Andy Yu-Guang Chen

1



Outline



- ◆ Problem formulation
- ◆ Bonus
- ◆ Requirements
- ◆ Report
- ◆ Grading
- ◆ Spice



2024/12/6

Andy Yu-Guang Chen

2



Outline



- ◆ **Problem formulation**
- ◆ Bonus
- ◆ Requirements
- ◆ Report
- ◆ Grading
- ◆ Spice



2024/12/6

Andy Yu-Guang Chen


3



 Problem formulation



- ◆ Design a 4-rows x 2-columns Digital CIM for Vector-Matrix Multiplications



2024/12/6

Andy Yu-Guang Chen

4

Problem formulation

◆ Inputs vector (I1, I2, I3, I4):

- I1, I2, I3, I4 are 4 bits (serially given from MSB to LSB)

◆ Weights matrix (W):

- 4 rows x 2 columns: $(W1, W2, W3, W4)_1, (W1, W2, W3, W4)_2$
- All weights are 4 bits (stored in latches by initial conditions)

◆ Output (O1, O2):

- O1, O2 are 10 bits
- $O1 = (I1 \times (W1)_1) + (I2 \times (W2)_1) + (I3 \times (W3)_1) + (I4 \times (W4)_1)$
- $O2 = (I1 \times (W1)_2) + (I2 \times (W2)_2) + (I3 \times (W3)_2) + (I4 \times (W4)_2)$




2024/12/6

Andy Yu-Guang Chen

5

Problem formulation

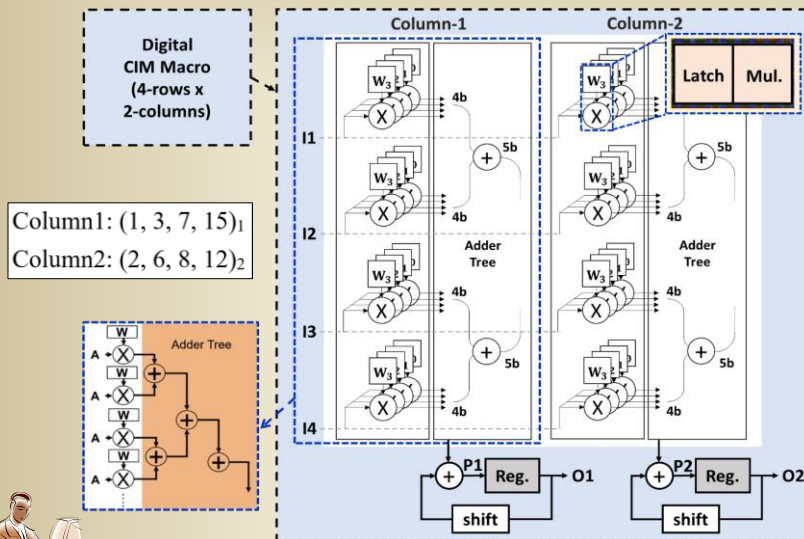

2024/12/6

Andy Yu-Guang Chen

6

Problem formulation

◆ Signals

Input signal	Bit width	Definition
I1, I2, I3, I4	1 bit each	Input serial signals
CLK	1 bit	Clock, period: 2 ns
RST	1 bit	Asynchronous active-low reset
IN_VAL	1 bit	Inputs are valid
Output signal	Bit width	Definition
O1, O2	10 bits each	Output signals
OUT_VAL	1 bit	O1 and O2 are valid (finished)
Other signal	Bit width	Definition
ii1, ii2, ii3, ii4	1 bit each	The input from flip-flop
P1, P2	10 bits each	The output before flip-flop


2024/12/6

Andy Yu-Guang Chen

7

Problem formulation

◆ Waveform

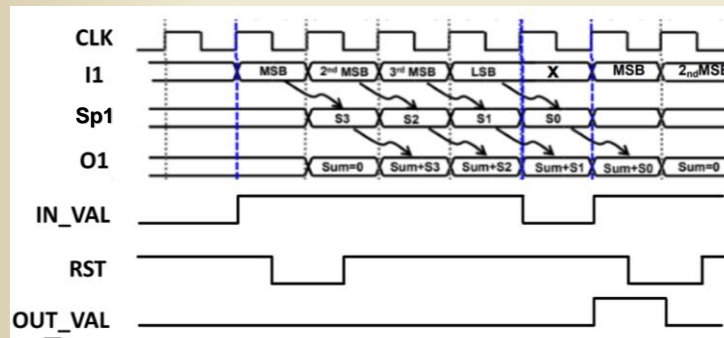

2024/12/6

Andy Yu-Guang Chen

8



Outline



- ◆ Problem formulation
- ◆ **Bonus**
- ◆ Requirements
- ◆ Report
- ◆ Grading
- ◆ Spice



2024/12/6

Andy Yu-Guang Chen

9



Bonus



- ◆ Design a 32-rows x 16-columns Digital CIM for Vector-Matrix Multiplications
- ◆ Same functionality of original version



2024/12/6

Andy Yu-Guang Chen

10



Outline

- ◆ Problem formulation
- ◆ Bonus
- ◆ **Requirements**
- ◆ Report
- ◆ Grading
- ◆ Spice



2024/12/6

Andy Yu-Guang Chen

11



Requirements

- ◆ Clock period in this program is set to 2 ns
- ◆ Rise and fall time will be 1 ps for all signals
- ◆ The operating voltage (VDD) is set to 1.8V, VSS is set to 0V, and the operating temperature is 30°C
- ◆ For transistors, set $L=0.18\mu\text{m}$, NMOS $W=0.36\mu\text{m}$, and PMOS $W=0.72\mu\text{m}$
- ◆ You must use the “cic018.l” to do this assignment, otherwise you will get 0 point



2024/12/6

Andy Yu-Guang Chen

12



Requirements

- ◆ Follow the naming rule below
 - SPICE code file name: DCIM.sp, DCIM_bonus.sp
 - Primary circuit name: DCIM
 - Cell name for your primary circuit: Xdcim
 - Signals in the program: named as we mention in page 7
- ◆ Complete this project using the process file provided by us. (on the ee-class)

```

*** call cell ***
Xdcim I1 I2 I3 I4 IN_VAL CLK RST O10 O11 O12 O13 O14 O15 O16 O17 O18 O19 O20 O21 O22 O23 O24 O25 O26 O27 O28 O29 OUT_VAL DCIM

*** DCIM block ***
.subckt DCIM I1 I2 I3 I4 IN_VAL CLK RST O10 O11 O12 O13 O14 O15 O16 O17 O18 O19 O20 O21 O22 O23 O24 O25 O26 O27 O28 O29 OUT_VAL
** Your code **

Xcontrol_in I1 I2 I3 I4 CLK RST i11 i12 i13 i14 INPUT_CON
Xcontrol_out1 P10 P11 P12 P13 P14 P15 P16 P17 P18 P19 CLK RST O10 O11 O12 O13 O14 O15 O16 O17 O18 O19 OUTPUT_CON
Xcontrol_out2 P20 P21 P22 P23 P24 P25 P26 P27 P28 P29 CLK RST O20 O21 O22 O23 O24 O25 O26 O27 O28 O29 OUTPUT_CON
.ends

```



2024/12/6

Andy Yu-Guang Chen

13



Outline

- ◆ Problem formulation
- ◆ Bonus
- ◆ Requirements
- ◆ **Report**
- ◆ Grading
- ◆ Spice



2024/12/6

Andy Yu-Guang Chen

14



Report

- ◆ The circuit diagram of your design and explaining your design (You can use screenshot to explain)
- ◆ The transistor level view of your CIM circuit and adder (You can just draw one of them and specified how you connect each)
- ◆ The bonus circuit if implemented
- ◆ Waveform of your simulation
- ◆ The delay and the power of the circuit
- ◆ The total number of transistors (NMOS and PMOS) you use in this program
- ◆ The hardness of this assignment and how you overcome it
- ◆ Any suggestions about this programming assignment



2024/12/6

Andy Yu-Guang Chen

15



Outline

- ◆ Problem formulation
- ◆ Bonus
- ◆ Requirements
- ◆ Report
- ◆ **Grading**
- ◆ Spice



2024/12/6

Andy Yu-Guang Chen

16



Grading

- ◆ Correctness (60%)
 - 5 test cases for each 12%
- ◆ Performance (20%): 5% (delay time) + 5% (power) + 10% (area)
 - Delay time and power by your simulation result
 - Area for your number of transistors in your program
 - Score function: $\text{maximum_score} * (\text{your result percentage of the class})$
 - Your performance score will be 0 if you failed the testcase.
- ◆ Readability of HSPICE code (10%)
- ◆ The report (20%)
- ◆ Bonus (10%)
 - 1 test case, the bonus score will be 10 if all correct, otherwise 0.



2024/12/6

Andy Yu-Guang Chen

17



Outline

- ◆ Problem formulation
- ◆ Bonus
- ◆ Requirements
- ◆ Report
- ◆ Grading
- ◆ Spice



2024/12/6

Andy Yu-Guang Chen

18



Initial condition

- ◆ To initialize the voltage.
- ◆ `.ic V(your_node_name)=voltage`

```
.ic V(W10)=1.8v
```
- ◆ If your node is not the global signal, you can access it by `sub_circuit_name.your_node_name`

```
.ic V(Xdcim.Xcim_c11.W0)=1.8v
```
- ◆ You can also initialize more than one node in one `.ic`

```
.ic V(Xdcim.Xcim_c11.W0)=1.8v V(Xdcim.Xcim_c11.W1)=0v
```



2024/12/6

Andy Yu-Guang Chen

19



Delay time

- ◆ Get the delay time from trigger signal to target signal (the first rising edge to half of voltage).
- ◆ `.measure TRAN element`
- ◆ `+TRIG V(trigger_signal) VAL=0.9 RISE=1`
- ◆ `+TARG V(target_signal) VAL=0.9 RISE=1`

```
.measure TRAN td
+ TRIG V(Xdcim.i11) VAL=0.9 RISE=1
+ TARG V(Xdcim.P10) VAL=0.9 RISE=1
```



2024/12/6

Andy Yu-Guang Chen

20



Power



- ◆ Get the average power of the circuit.
- ◆ `.measure TRAN element AVG POWER`

```
.measure TRAN pwr AVG POWER
```



2024/12/6

Andy Yu-Guang Chen

21



Simulation results



- ◆ You can find the simulation results in `.lis` file
- ◆ Delay time & power

```
***** transient analysis tnom= 25.000 temp= 30.000 *****
td= 243.3594p  targ= 4.3664n  trig= 4.1231n
pwr= 821.6744u  from= 0.      to= 20.0000n
```

- ◆ Number of transistor

```
***** Circuit Statistics *****
# nodes      = 2683 # elements = 1105
# resistors  = 0 # capacitors = 0 # inductors = 0
# mutual_inds = 0 # vccs      = 0 # vcvs      = 0
# cccs       = 0 # ccvs      = 0 # volt_srcs = 8
# curr_srcs  = 0 # diodes    = 0 # bjts      = 0
# jfets      = 0 # mosfets   = 1097 # U elements = 0
# T elements = 0 # W elements = 0 # B elements = 0
# S elements = 0 # P elements = 0 # va device = 0
# vector_srcs = 0 # N elements = 0
```



2024/12/6

Andy Yu-Guang Chen

22