

黃偉祥 X1136010

Limitations:

VDD = 1.8v
L = 0.18um
W >= 0.25um

Settings:

pFET(w=0.5u),nFET(w=0.25u), .tem=30
h1.sp : .tran 0.01n 260n
h1_bonus.sp : .tran 0.01n 520n

How to perform the simulation

1. Enter the command below to switch to hspice.chsrc, it will give you the hspice version
 - source /usr/cad/synopsys/CIC/hspice.chsrc
2. Use hspice to compile your .sh file and output as .lis file
 - hspice -i input.sh -o output.lis
3. If the last line showed **hspice job concluded** then you are good to go and check the waveview. But if showed aborted or something else then you need to check the error message in .lis file

For example:


```
[tsx1136010@linuxcad30 ~]$ source /usr/cad/synopsys/CIC/hspice.chsrc
set hspice version: 2020.12 (default)
[tsx1136010@linuxcad30 ~]$ hspice -i h1
h1.sp          h1/          h1_bonus.sp
[tsx1136010@linuxcad30 ~]$ hspice -i h1.sp -o ./h1/h1.lis
Using: /home/tools/synopsys/hspice/2020.12/hspice/linux64/hspice -i 'h1.sp' -o
./h1/h1.lis

>info:          ***** hspice job concluded
```

 4. Enter the command below to switch to source customexplorer.chsrc, it will give you customerexplorer version
 - source /usr/cad/synopsys/CIC/customexplorer.chsrc
5. Use custom waveview to check your result wave, using wv target_file.tr0
 - wv file.tr0

For example:

```
[tsx1136010@linuxcad30 ~]$ !76
source /usr/cad/synopsys/CIC/customexplorer.cshrc
set customexplorer version: 2020.12 (default)
[tsx1136010@linuxcad30 ~]$ ls
bonus h1 h1_bonus.sp h1.sp mylib.sp
[tsx1136010@linuxcad30 ~]$ cd h1
[tsx1136010@linuxcad30 ~/h1]$ ls
h1.ic0 h1.st0 inv.lis inv.tr0 sxcmd.log.2
h1.lis h1.tr0 inv.pa0 sxcmd.log sxcmd.log.3
h1.pa0 inv.ic0 inv.st0 sxcmd.log.1 sx_crash.sx
[tsx1136010@linuxcad30 ~/h1]$ wv h1.tr0
█
```




6. Drag the thing into waveview window then you can see all wave of your program, you can delete the useless wave and ungroup some of them to have a clean view.

For example:


- We can see the **output** will be **high** only when **both inputs** are **high**, which is the AND gate function.

3. OR2 gate waveform

 

- We can see the **output** will be **low** only when **both inputs** are **low**, which is the OR gate function.

4. The specific logic function

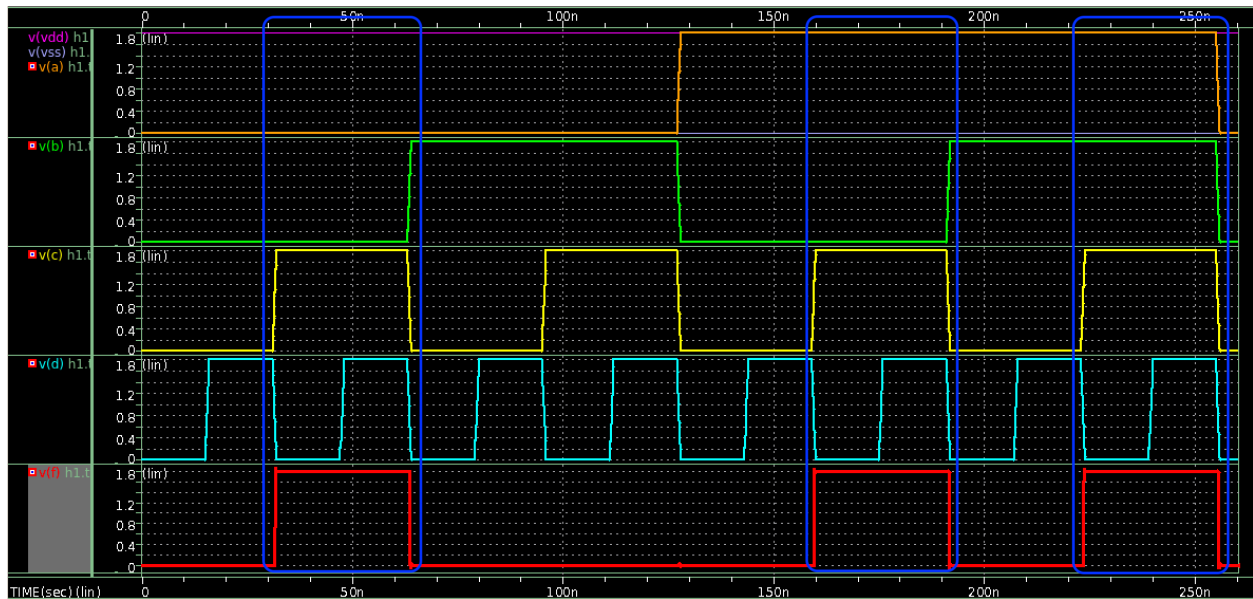

| a | b | c | $(c \wedge (\neg b \vee a))$ |
|---|---|---|------------------------------|
| F | F | F | F |
| F | F | T | T |
| F | T | F | F |
| F | T | T | F |
| T | F | F | F |
| T | F | T | T |
| T | T | F | F |
| T | T | T | T |

| a | b | c | d | $((d \wedge \neg(b \vee \neg c)) \vee (c \wedge (\neg b \vee a)))$ |
|---|---|---|---|--|
| F | F | F | F | F |
| F | F | F | T | F |
| F | F | T | F | T |
| F | F | T | T | T |
| F | T | F | F | F |
| F | T | F | T | F |
| F | T | T | F | F |
| F | T | T | T | F |
| T | F | F | F | F |
| T | F | F | T | F |
| T | F | T | F | T |
| T | F | T | T | T |
| T | T | F | F | F |
| T | T | F | T | F |
| T | T | T | F | T |
| T | T | T | T | T |

- From the true table, we can know that **output** will be **high** only when **a,b,c** = $\{(0,0,1), (1,0,1), (1,1,1)\}$
 - o True table from Truth Table Generator
(<https://web.stanford.edu/class/cs103/tools/truth-table-tool/>)

This is my prove:

$$\begin{aligned}
 F &= d \cdot \overline{(b + \bar{c})} + c(\bar{b} + a) \\
 &= d \cdot (\bar{b} \cdot \bar{\bar{c}}) + c(\bar{b} + a) \\
 &= d \cdot \bar{b} \cdot c + c\bar{b} + ac \\
 &= c(d\bar{b} + \bar{b} + a) \\
 &= c(\bar{b} + a)
 \end{aligned}$$

$a + ab = a$
 $a(1 + b) = a$

The hardness of this assignment and how you overcame it

1. Mac m1 cannot use MobaXterm and default mac terminal can only connect to workstation but cannot open waveview

```
[tsx1136010@linuxcad30 ~/h1]$ source /usr/cad/synopsys/CIC/h
hercules.cshrc* hsimplus.cshrc* hspice.cshrc*
[tsx1136010@linuxcad30 ~/h1]$ source /usr/cad/synopsys/CIC/hspice.cshrc
set hspice version: 2020.12 (default)
[tsx1136010@linuxcad30 ~/h1]$ hspice -i h1.sp -o h1.lis
Using: /home/tools/synopsys/hspice/2020.12/hspice/linux64/hspice -i 'h1.sp' -o h1.lis

>info:          ***** hspice job concluded
[tsx1136010@linuxcad30 ~/h1]$ source /usr/cad/synopsys/CIC/cus
customcompiler.cshrc* customexplorer.cshrc*
[tsx1136010@linuxcad30 ~/h1]$ source /usr/cad/synopsys/CIC/customexplorer.cshrc
set customexplorer version: 2020.12 (default)
[tsx1136010@linuxcad30 ~/h1]$ wv h1.tr0 &
[1] 21407
[tsx1136010@linuxcad30 ~/h1]$ Fatal: QXcbConnection: Could not connect to display (:0, )
```

- I found an alternative software for mac m1 which is XQuartz (<https://www.xquartz.org/releases/XQuartz-2.8.5.html>)
 - i. `ssh -X ts_stuID@server_ip -p 22`
- 2. Logic function too complicated, so I simplified the logic function.

$$\begin{aligned} F &= d \cdot \overline{(b + \bar{c})} + c(\bar{b} + a) \\ &= d \cdot (\bar{b} \cdot \bar{\bar{c}}) + c(\bar{b} + a) \\ &= d \cdot \bar{b} \cdot c + c\bar{b} + ac \\ &= c(d\bar{b} + \bar{b} + a) \\ &= c(\bar{b} + a) \end{aligned}$$

$$\begin{aligned} a + ab &= a \\ a(1 + b) &= a \end{aligned}$$

3. When I'm doing bonus I don't want to rewrite all the basic gates again, so I copy "h1.sp" without the simulation part as "mylib.sp".

```
[(base) wongweixiang@Wongs-MacBook-Air circuit_hw1 % cat mylib.sp
** X1136010_HW1 **
** Environment setting **
*****
.protect
.lib "/usr/cad/cic018.1" tt
.unprotect

Cdecap vdd vss 0.1u

*** Inverter ***
.subckt INV in1 out vdd vss
**pFET drain=output, gate=input, source and body = vdd **
mp1 out in1 vdd vdd P_18 w=0.5u l=0.18u
**nFET drain=output, gate=input, source and body = vss(gnd) **
mn1 out in1 vss vss N_18 w=0.25u l=0.18u
.ends

*** NOR ***
.subckt NOR2 in1 in2 NOR vdd vss
** 2 pFET in series **
mp1 pd1 in1 vdd vdd P_18 w=0.5u l=0.18u
mp2 NOR in2 pd1 vdd P_18 w=0.5u l=0.18u
** 2 nFET in parallel **
mn1 NOR in1 vss vss N_18 w=0.25u l=0.18u
mn2 NOR in2 vss vss N_18 w=0.25u l=0.18u
.ends

*** OR ***
.subckt OR2 in1 in2 OR vdd vss
Xnor in1 in2 NOR vdd vss NOR2
** NOR&INV = OR **
Xinv NOR OR vdd vss INV
.ends





*** NAND ***
.subckt NAND2 in1 in2 NAND vdd vss
** 2 pFET in parallel **
mp1 NAND in1 vdd vdd P_18 w=0.5u l=0.18u
mp2 NAND in2 vdd vdd P_18 w=0.5u l=0.18u
** 2 nFET in series **
mn1 NAND in1 ns1 vss N_18 w=0.25u l=0.18u
mn2 ns1 in2 vss vss N_18 w=0.25u l=0.18u
.ends

*** AND ***
.subckt AND2 in1 in2 AND vdd vss
Xnand in1 in2 NAND vdd vss NAND2
Xinv NAND AND vdd vss INV
.ends

*** logic function ***
.subckt logic A B C D F_out vdd vss
Xinv B B_ vdd vss INV
Xor A B_ f1 vdd vss OR2
Xand C f1 F_out vdd vss AND2
.ends
(base) wongweixiang@Wongs-MacBook-Air circuit_hw1 %
```


Bonus – MUX 4 to 1

- transistor-based schematic diagram

    


MUX 4 to 1 waveforms

1. $S1=0, S0=0$

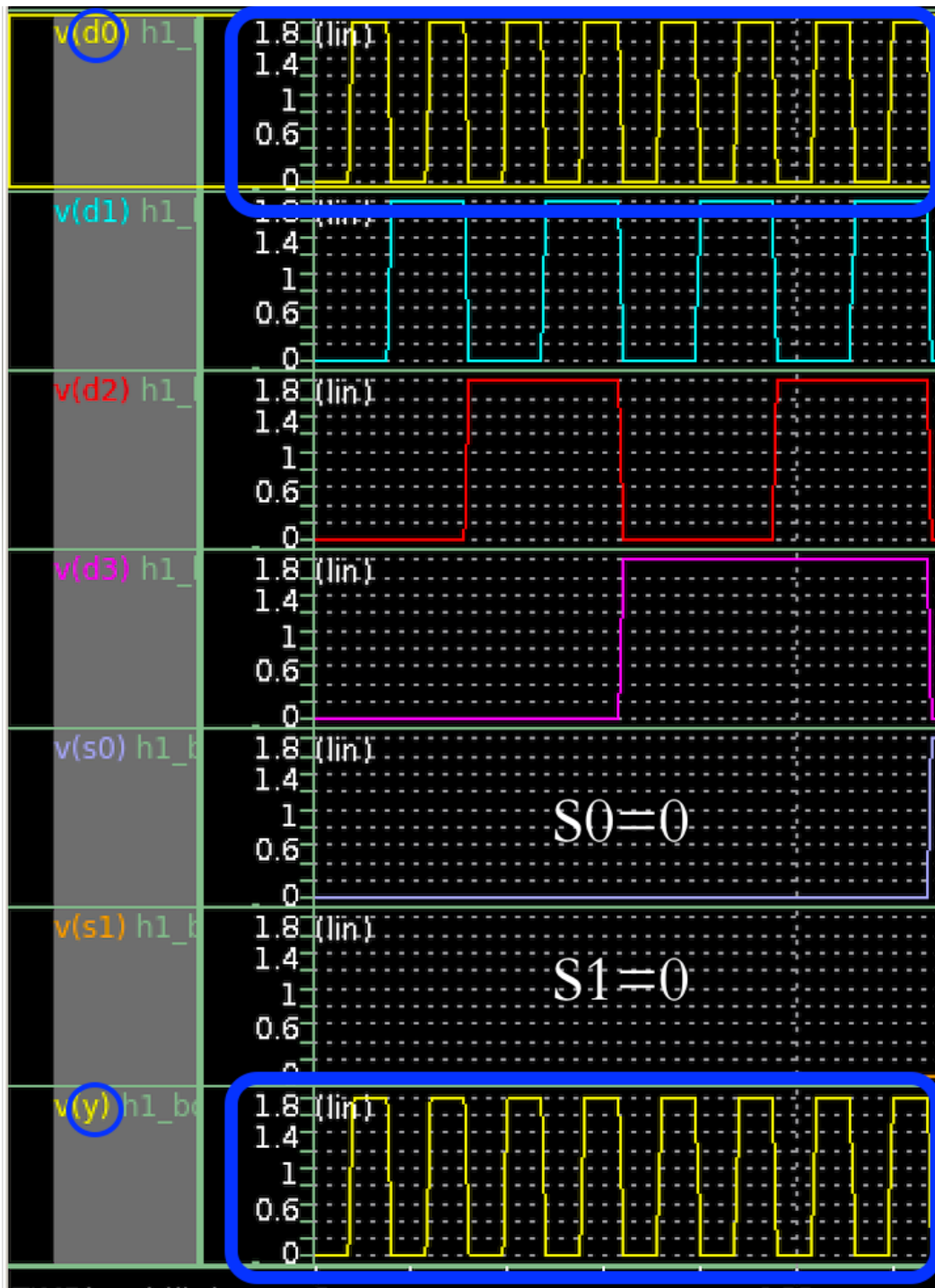


- When $S0$ and $S1$ are both equal to 0, output will same as $D0$.

2. $S1=0, S0=1$

 


- When $S1 = 0$ and $S0 = 1$, output will same as $D1$.

3. $S1=1, S0=0$

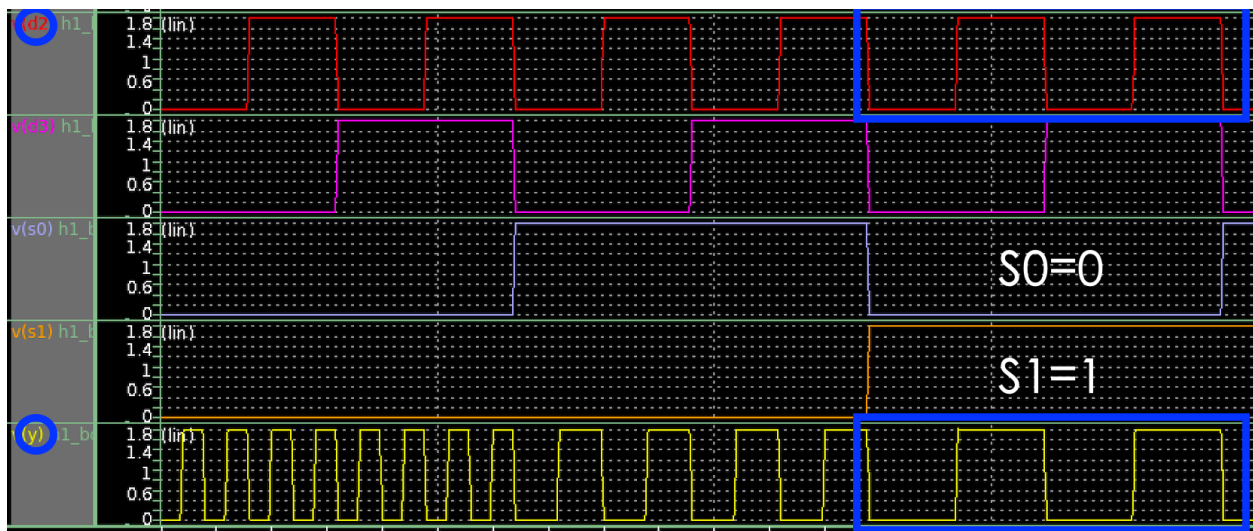

- When $S1 = 1$ and $S0 = 0$, output will same as $D2$.

4. $S1=1, S0=1$

 

- When **S1** = 1 and **S0** = 1, output will same as **D3**.

Full wave for 520n

